



Basic Capacitance Measurement Technique

Isolate the safety grounds on the power plugs of both the oscilloscope and the waveform generator

Use the "Time Constant" formula $t = RC$ to solve for capacitance
Capacitance in FARADS, time in SECONDS and resistance in OHMS

Compute Capacitance with Sq Wave Gen and Scope

- Demonstrate how to measure capacitance with this setup
- Measure "time" in seconds at 63.2% of waveform height
- Place time and resistance in formula - pop capacitance
- Verify capacitance with Fluke 87-V
- Note the use of low frequencies: 340 Hz, 80Hz, 0.100Hz
- Other capacitor values you'll have to hunt for the correct Freq/Res comb.
- For CONSTANT VOLTAGE maintain a square wave on CH 2
- ESR does not upset this measurement *unless it is a large % of R*
- Vs can be any voltage!** Adjust Vs or scope for 10 scope div.

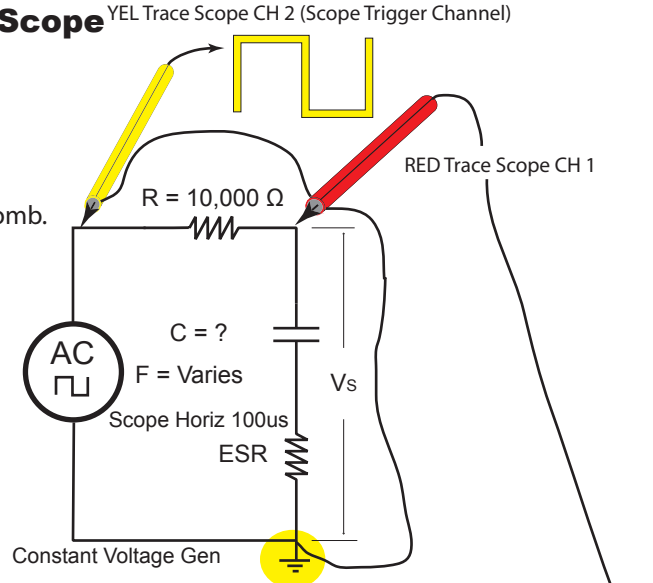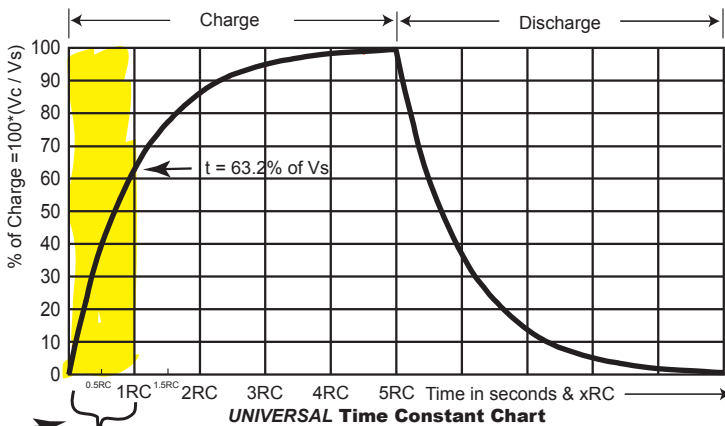

$$C = t / R \text{ (for 1 time constant)}$$

"t" is Measured from 0 to 63.2% of Vs

Time Interval to Measure (1 "time constant")

Place a **0.015uf** capacitor in the test circuit.

Adjust the scope horiz and vertical & wave form gen until a "tooth" pattern is observed.

Measure the TIME in SECONDS from the beginning of the "tooth" waveform to 63.2% of Vs (1 time constant).

$$t = 0.000150S \quad C = t / R \text{ (for 1 time constant)} = 0.000150s / 10,000 \Omega = 0.0000000150F = 0.0150uf$$

Place a **0.100uf** capacitor in the test circuit. Re-adjust Frequency and vertical gain for "Tooth" pattern.

$$t = 0.00100S \quad C = t / R \text{ (for 1 time constant)} = 0.00100s / 10,000 \Omega = 0.000000105F = 0.100uf$$

Place a **180uf** capacitor in the test circuit. **Reduce R to 5000 Ohms**. Re-adjust Frequency and vertical gain for "Tooth" pattern.

$$t = 0.900S \quad C = t / R \text{ (for 1 time constant)} = 0.900s / 5,000 \Omega = 0.000180F = 180uf$$

Examples Equipment Setup:

Scope Settings for: **0.015uf**
Horiz: 500us 100us
CH1: DC X1 1V/div
CH2: DC X1 5V/div Trigger
R = 10,000 Ohms

Waveform Gen: State 2
Output Square High Z
F = 340 Hz
VPPgen = 9.800
Acquire Mode: Average 16
Acquire Length: 1K

Scope Settings for: **0.10uf**
Horiz: 2ms 500us
CH1: DC X1 1V/div
CH2: DC X1 5V/div Trigger
R = 10,000 Ohms

Waveform Gen: State 3
Output Square High Z
F = 80 Hz
VPPgen = 9.800

Scope Settings for: **180uf**
Horiz: 500ms
CH1: DC X1 200mv/div
CH2: DC X1 1V/div Trigger
R = **5,000 Ohms**

Waveform Gen: State 4
Output Square High Z
F = 0.100 Hz
VPPgen = 3.400
Acquire mode: Sample Acquire Length: 10M